

# Lesson 4: Logic Gates & Boolean Algebra

## 1. Logic Gates

### Gate Lexicon

Gate	Expression	Output is 1 when...
NOT	$L = \overline{A}$	input is 0.
AND	$L = A \cdot B$	all inputs are 1.
OR	$L = A + B$	at least one input is 1.
NAND	$L = \overline{A \cdot B}$	any input is 0.
NOR	$L = \overline{A + B}$	all inputs are 0.
XOR	$L = A \oplus B$	inputs are different.
XNOR	$L = \overline{A \oplus B}$	inputs are the same.

### Universal Gates (NAND & NOR)

- **Why universal?** Any logic gate can be constructed using only NAND gates or only NOR gates. This makes manufacturing ICs cheaper and simpler.

### Implementations with NAND

- **NOT A** =  $(A \cdot A)'$
- **A AND B** =  $((A \cdot B)')'$
- **A OR B** =  $(A' \cdot B')'$

## 2. Boolean Algebra

### Key Laws & Theorems

- **Identity:**  $A + 0 = A$ ,  $A \cdot 1 = A$
- **Complement:**  $A + \overline{A} = 1$ ,  $A \cdot \overline{A} = 0$
- **Commutative:**  $A + B = B + A$
- **Associative:**  $A + (B + C) = (A + B) + C$
- **Distributive:**  $A(B + C) = AB + AC$
- **De Morgan's:**
  - $\overline{A \cdot B} = \overline{A} + \overline{B}$
  - $\overline{A + B} = \overline{A} \cdot \overline{B}$
- **Redundancy:**  $A + \overline{A}B = A + B$

## 3. Standard Forms

### SOP & POS

- **SOP (Sum of Products):** Sum of AND terms (Minterms). Derived from rows where output is 1.
  - Ex:  $F = \overline{A}BC + A\overline{B}C$
- **POS (Product of Sums):** Product of OR terms (Maxterms). Derived from rows where output is 0.
  - Ex:  $F = (A + B + C)(A + \overline{B} + C)$

### Deriving SOP from a Truth Table

A	B	C	F	Minterm
0	0	0	0	
0	0	1	1	$\rightarrow \overline{A}\overline{B}C$
0	1	0	0	
0	1	1	1	$\rightarrow \overline{A}BC$
...	...	...	...	

**SOP Expression:**  $F = \overline{A}\overline{B}C + \overline{A}BC$

## 4. Karnaugh Maps (K-Maps)

### Simplification Rules

1. Group only 1s, never 0s.
2. Groups must be rectangular & contain a power of 2 number of cells (1, 2, 4, 8...).
3. No diagonal groups.
4. Make groups as large as possible.
5. Groups can overlap. Wrap-around is allowed.
6. Use the fewest number of groups possible.

### 3-Variable K-Map Example

**Simplify**  $F = \overline{A}\overline{B}C + \overline{A}BC + A\overline{B}C + A\overline{B}\overline{C}$

#### 1. Map the 1s:

	AB			
C	00	01	11	10
0				1
1	1	1		1

#### 2. Group the 1s: Two groups are made.

- Group 1 (Green): The two 1s in column AB=10. This simplifies to  $A\overline{B}$ .
- Group 2 (Blue): The two 1s in row C=1, columns AB=00 and AB=01. This simplifies to  $\overline{A}C$ .

#### 3. Final Expression: $F = A\overline{B} + \overline{A}C$

## 5. Circuit Types

### Combinational vs. Sequential

- **Combinational Circuits:**
  - Output depends **only** on the current inputs.
  - Has **no memory**.
  - Examples: Adders, Decoders.
- **Sequential Circuits:**
  - Output depends on current inputs **and** past states.
  - Has **memory** to store past states.
  - Uses a **feedback loop** (output is fed back as an input).
  - Examples: Flip-Flops, Counters.

## 6. Practical Circuits

### Adders

- **Half Adder:** Adds 2 bits.
  - **Sum** =  $A \oplus B$
  - **Carry** =  $A \cdot B$
- **Full Adder:** Adds 3 bits (A, B,  $C_{in}$ ). Built with two Half Adders and an OR gate.
  - **Sum** =  $A \oplus B \oplus C_{in}$
  - **Carry Out** =  $A \cdot B + C_{in}(A \oplus B)$

### Memory

- **Flip-Flop:** The basic building block of memory. A sequential circuit that can **store** a single bit (0 or 1).
- **RS Latch (Flip-Flop):** Simplest type, built with cross-coupled NAND or NOR gates. Has Set (S) and Reset (R) inputs.

### Design Example: Simple Alarm

**Problem:** An alarm (F) should sound if a sensor (A) is triggered, but only if the system is armed (B) and the door is closed (C).

1. **Truth Table:** The only time F=1 is when A=1, B=1, and C=1.
2. **Expression:** The SOP expression is simply the minterm for that one case:  $F = A \cdot B \cdot C$ .
3. **Circuit:** A single 3-input AND gate.